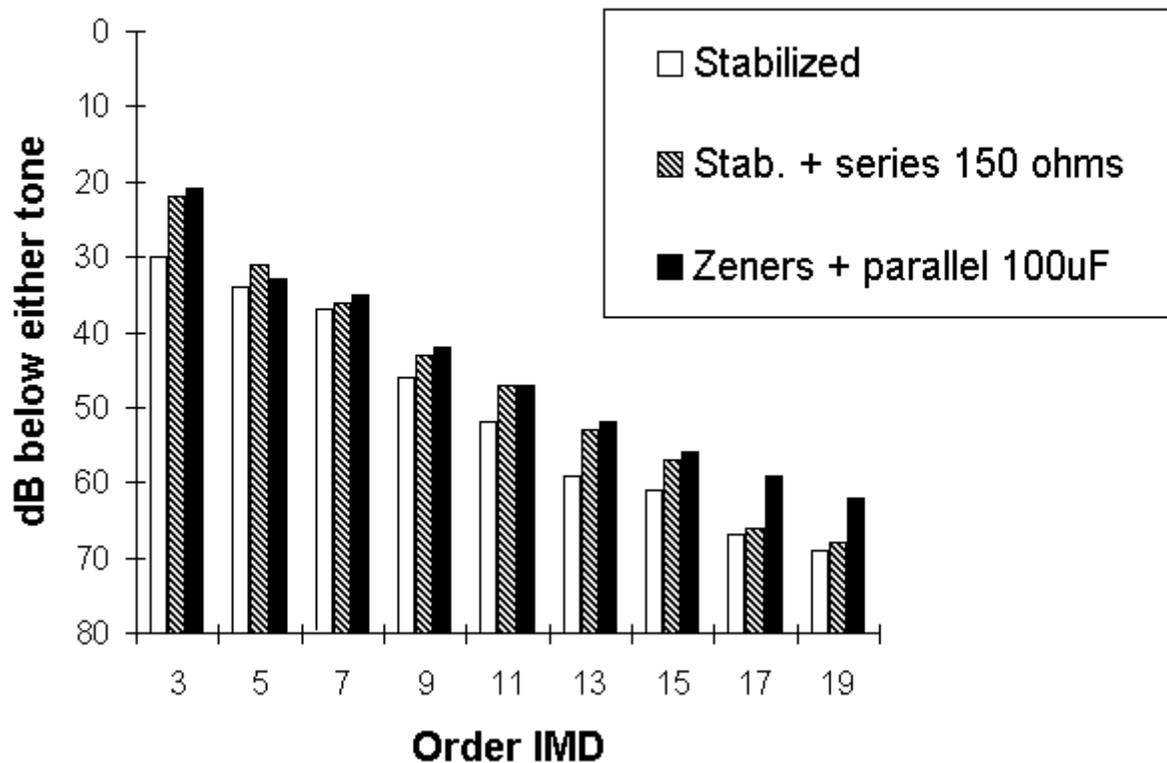


Lower IMD from Tetrode Power Amplifiers

John Nelson, GW4FRX has been a constant campaigner for cleaner signals, and has been responsible for many key developments in tetrode power supplies (see Chapters 6 and 11 of [The VHF/UHF DX Book](#)). This bar-chart shows his measurements of two-tone IMD performance of a pair of 4CX250Rs in class AB1 at 500W PEP output, with three different types of screen supply.

IMD for various screen supplies (GW4FRX)



Test conditions

- Two Eimac 4CX250Rs, operating (heater) time 4500hrs
- Va 2000V
- Vg2 350V
- Zero-signal anode current 100mA per tube
- Two-tone test signal, 1kHz spacing, class-AB1 drive conditions (no g1 current).

1. Amplifier tuned and loaded initially for -30dB 3rd-order IMD at 500W output, using GW4FRX stabilized screen supply (350V). IMD measured.
2. 150 ohms series resistance added to screen supply to simulate poorer regulation. IMD re-measured.
3. Screen supply replaced by 350V zeners with 100uF in parallel to improve audio-frequency regulation. IMD re-measured.

[See comments below](#)

Comments

- **The best IMD performance** (white bars) came from GW4FRX's own extremely well regulated supply. This has excellent DC stability and a very low dynamic impedance at all audio frequencies, from 3kHz down to syllabic frequencies of a few hertz.
- **Second best** (checkered bars) was the highly stabilized supply with a 150-ohm series resistor added to artificially increase the output

impedance.


- **A poor third** (black bars) – especially for higher-order IMD – is the traditional 'chain of zeners' stabilizer with a 100uF parallel reservoir capacitor.

Conclusions

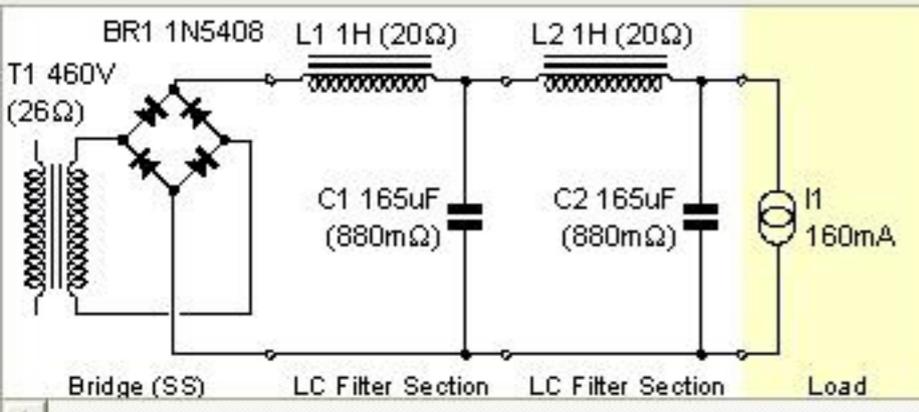1. A screen voltage regulator with low dynamic impedance **at all audio frequencies from 3kHz down to syllabic frequencies of a few hertz** will produce significantly better IMD performance, especially for the higher-order products that make your signal 'wide'.
2. Improved screen stabilization can give IMD performance that is notably better than stated in the Eimac data sheets.
3. **Zener stabilizers are no longer state-of-the-art.**


On the air, these conclusions have been verified by many British and European stations. Tight screen voltage regulation really does make a difference to your reputation!


Back to [G3SEK's Amateur Radio Technical Notebook](#)



Simulate For 6 000 ms after a reporting delay of 0 S


Result	Min	Max	
<input type="checkbox"/> I(BR1)	-3,1557m	3,8576	3,1
<input type="checkbox"/> I(C1)	-427,93m	2,9259	3,1
<input type="checkbox"/> I(C2)	-305,20m	2,9910	3,1
<input type="checkbox"/> I(I1)	0	160m	1
<input type="checkbox"/> I(L1)	-3,1657m	4,1553	4,1
<input type="checkbox"/> I(L2)	-145,20m	3,1510	3,1
<input type="checkbox"/> I(T1)	-4,1553	3,8576	8,1
<input type="checkbox"/> V(BR1)	-2,6635k	48,025	2,7
<input type="checkbox"/> V(C1)	0	522,83	52
<input type="checkbox"/> V(C2)	-152,92m	510,72	51
<input checked="" type="checkbox"/> V(I1)	-152,92m	510,72	51
<input type="checkbox"/> V(L1)	-522,51	2,1581k	2,6
<input type="checkbox"/> V(L2)	-109,17	245,25	3E
<input type="checkbox"/> V(T1)	-646,09	645,98	1,2

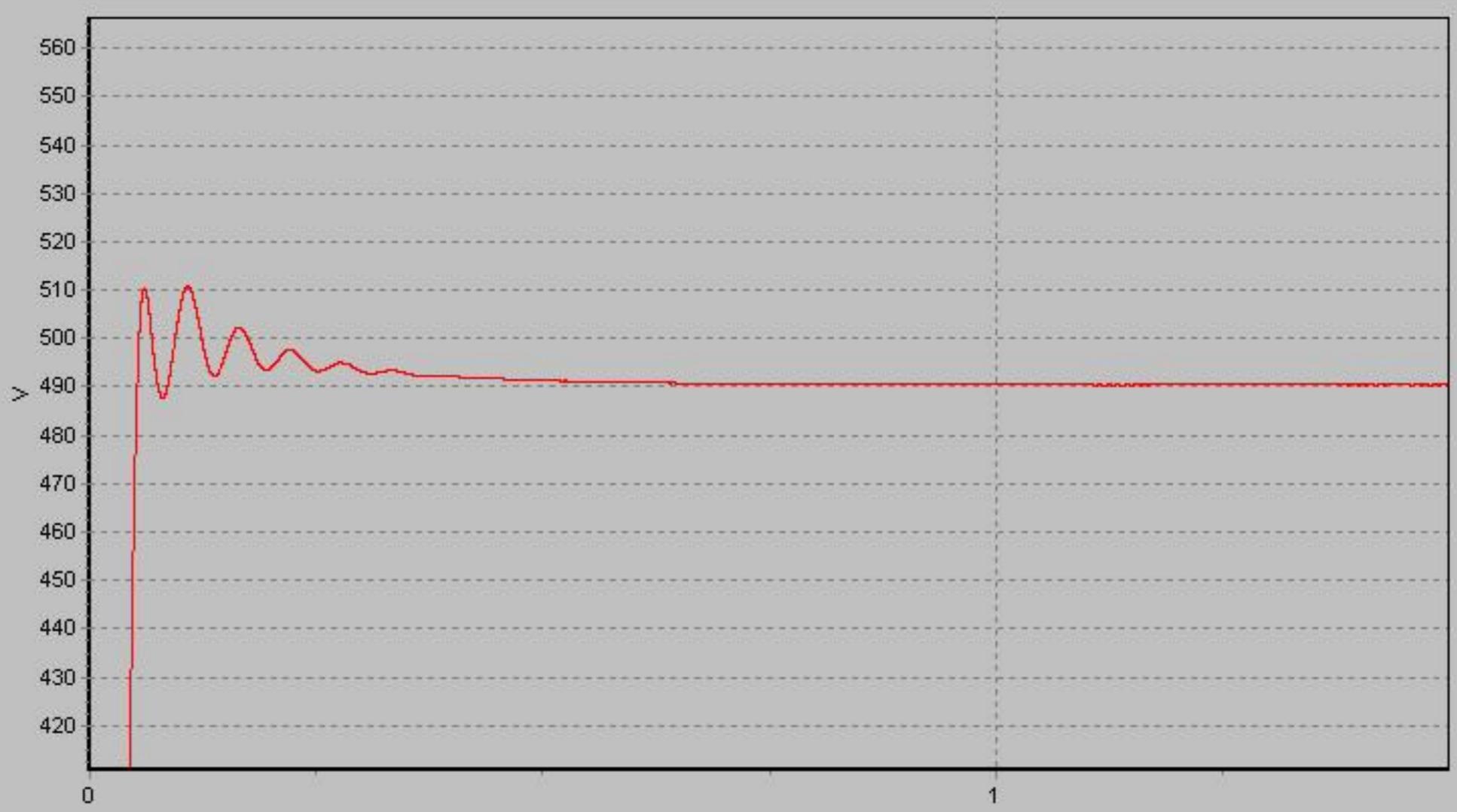

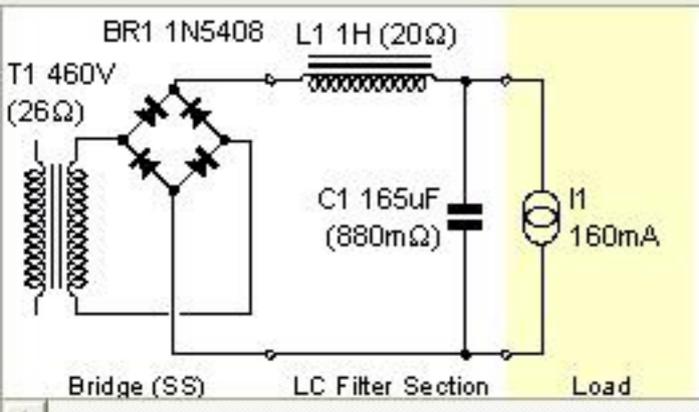

Simulate For 6 000 ms after a reporting delay of 0 s

Result	Min	Max	
<input type="checkbox"/> I(BR1)	-3,1617m	3,5667	3,1
<input type="checkbox"/> I(C1)	-163,16m	3,9585	4,
<input type="checkbox"/> I(I1)	0	160m	1
<input type="checkbox"/> I(L1)	-3,1626m	4,1185	4,
<input type="checkbox"/> I(T1)	-4,1185	3,5667	7,
<input type="checkbox"/> V(BR1)	-2,7060k	47,198	2,7!
<input type="checkbox"/> V(C1)	-152,64m	558,72	5E
<input checked="" type="checkbox"/> V(I1)	-152,64m	558,72	5E
<input type="checkbox"/> V(L1)	-563,05	2,1599k	2,7.
<input type="checkbox"/> V(T1)	-647,51	647,80	1,2!

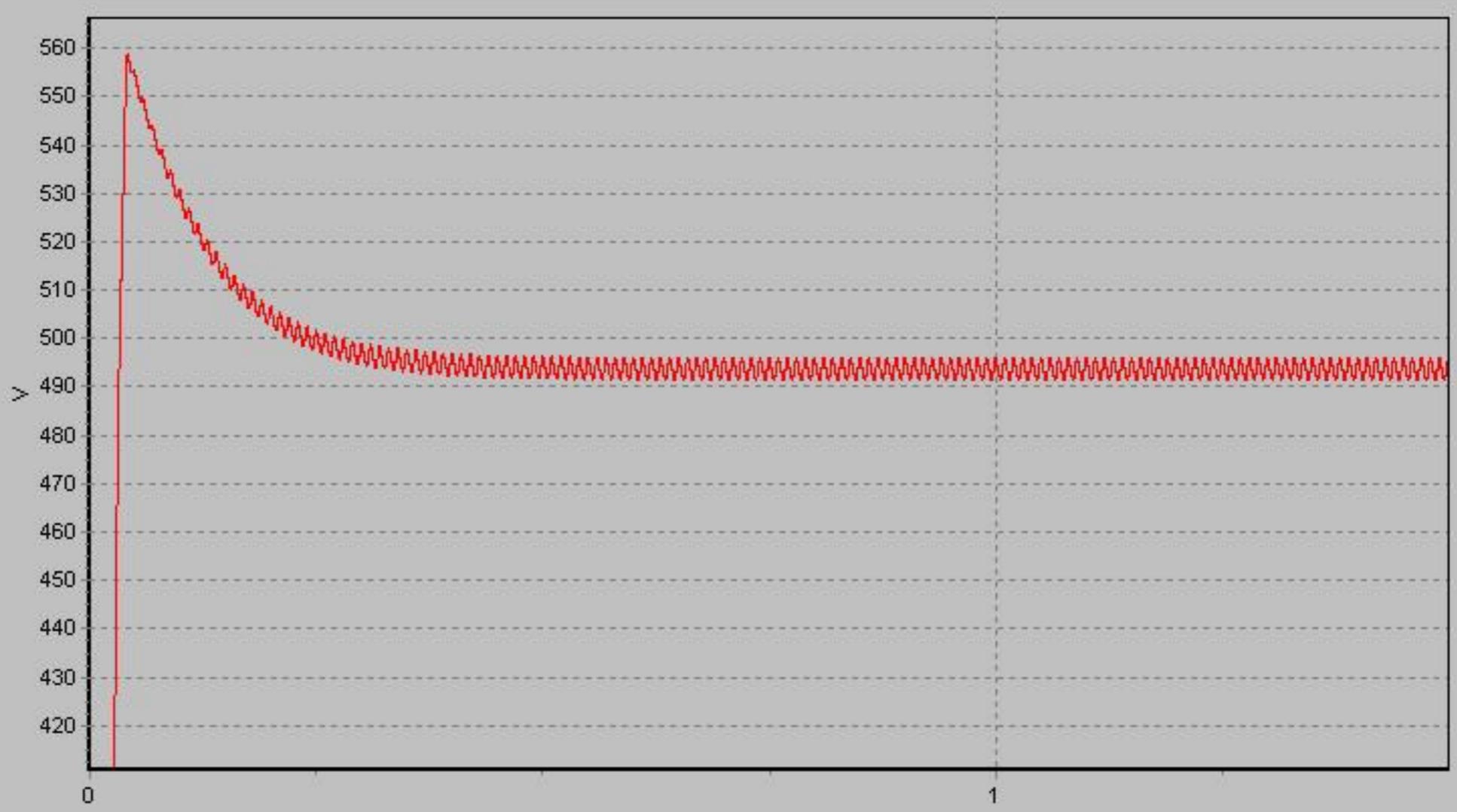

- V(I1)

