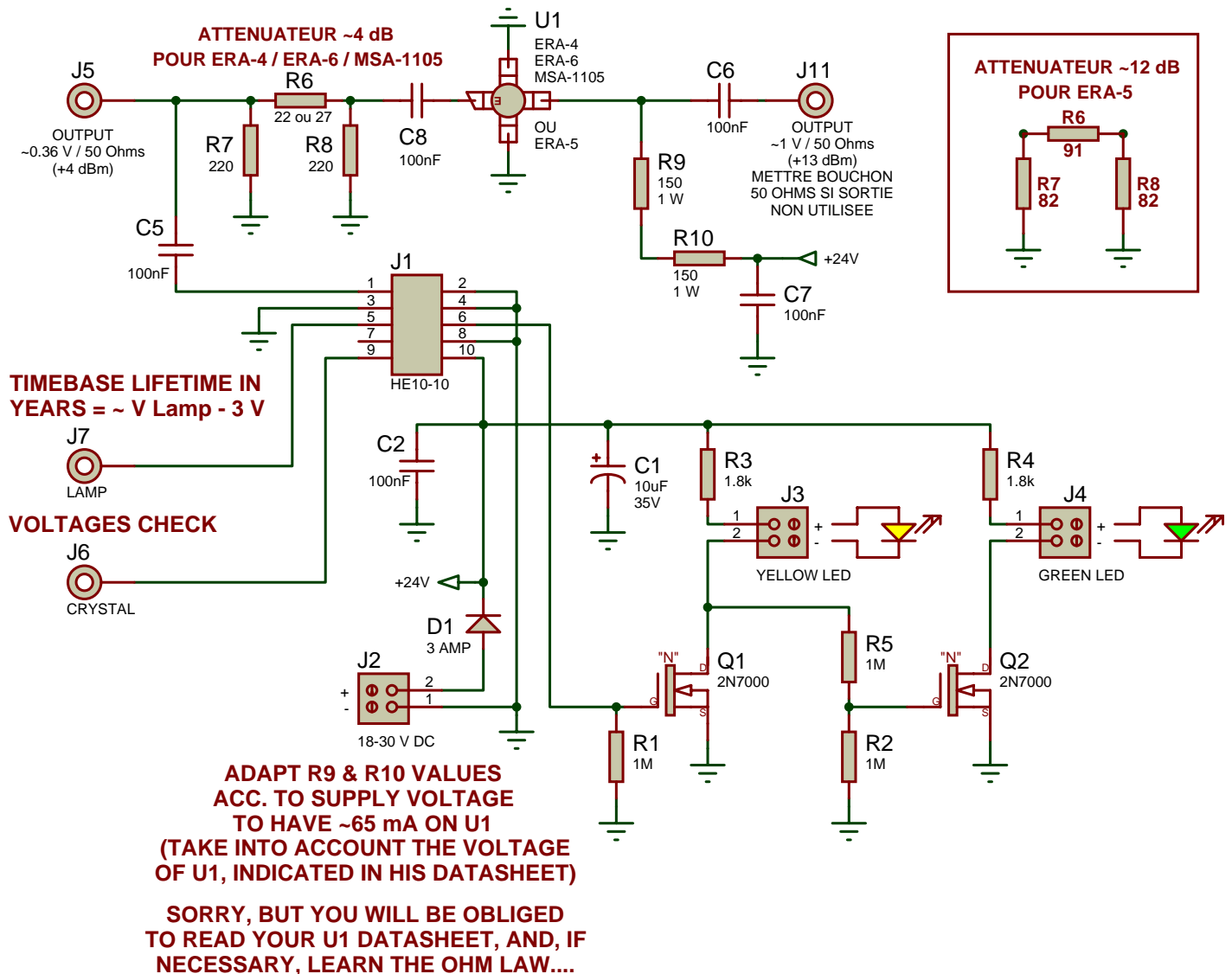


10 MHZ RUBIDIUM EFRATOM LPRO-101 SIMPLIFIED INTERFACE


DATE:13/01/12 REV:3a PAGE: 1/1
BY: f1frv@sfr.fr
DOC N°: AMATEUR RADIO

IF 0.55 V OUT IS ENOUGH FOR YOU, NO NEED FOR U1 AND RELATED COMPONENTS



ZERO BEAT COMPARISON BETWEEN 2 OSCILLATORS TO BE USED FOR ADJUSTMENT AGAINST A MORE ACCURATE REFERENCE

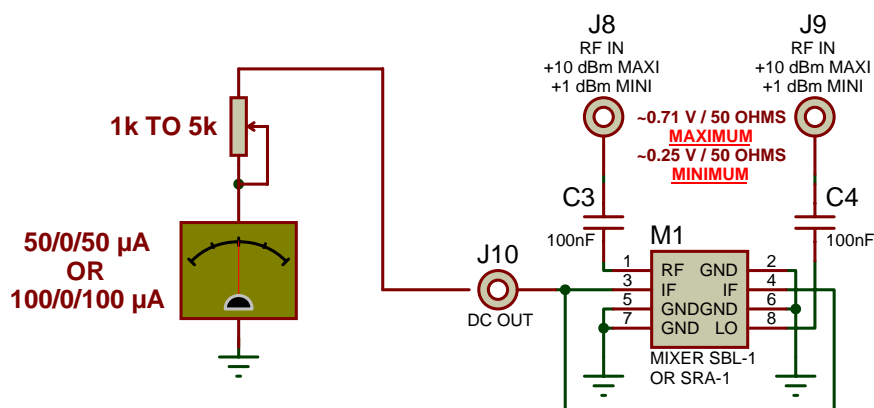THIS IDEA IS TAKEN FROM F6ETI WEB SITE. FOR EXPLANATIONS (IN FRENCH), SEE:
<http://pagesperso-orange.fr/ph-martin/f6eti/realisations/rubidium/index.htm>



10 MHz RUBIDIUM EFRATOM LPRO-101 SIMPLIFIED INTERFACE

DATE: January 2012 REV: 3a
BY: F1FRV@SFR.FR
DOC Nr: AMATEUR RADIO

WITH ZERO BEAT MIXER

